

CMPSCI 105: Lecture #4 Gates and Truth Tables

©2014 Dr. William T. Verts

First, an aside: Binary Addition

- Since numbers can be converted between bases, addition in one base gives the same answer as addition in another base,
- Adding in binary is simpler than adding in decimal,
- So we build computers to add in binary rather than in decimal!

©2014 Dr. William T. Verts

Binary Addition Table

+	0	1
0	0	1
1	1	10

Zero, with a Carry

©2014 Dr. William T. Verts

Example

. ← Carries
 0110010101000101
 +0110011100010110
 1100110001011011

©2014 Dr. William T. Verts

Now back to Logic...

©2014 Dr. William T. Verts


When is the sentence True?

- “I am going to the store and going to the beach”
- Clause A: “going to the store”
- Clause B: “going to the beach”
- Either may independently be True or False.
- When is the overall sentence True?
- Only when both are True.

©2014 Dr. William T. Verts

When does Water flow?


- When both valves are open

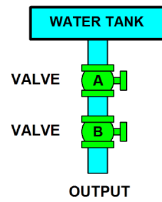

©2014 Dr. William T. Verts

When does the light come on?

- When both switches are closed

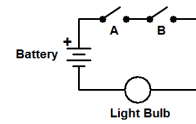

©2014 Dr. William T. Verts

Commonalities

- In all three cases the underlying logic is the same:
 - Both clause A and clause B must be True for the sentence to be True.
 - Both Valve A and Valve B must to open for water to flow.
 - Both Switch A and Switch B must be closed for the light bulb to come on.
- The only thing in common is **AND**.

©2014 Dr. William T. Verts

Truth Tables

- A **Truth Table** is a tabular way of describing all possible behaviors for a binary system.
- We could use T and F to indicate True and False, but instead we will define 1 for True and 0 for False.
- The number of rows in a Truth Table is 2 raised to the power of the number of inputs.

©2014 Dr. William T. Verts

Truth Table for AND (two inputs)

A	B	AND
0	0	0
0	1	0
1	0	0
1	1	1

©2014 Dr. William T. Verts

Can we have more than Two inputs?

- YES.**
- "I am going to the store and going to the beach and going to the movies."
- The pipe contains three valves in series, **all** must be open for water to flow.
- The circuit contain three switches in series, **all** must be closed for the light bulb to come on.

©2014 Dr. William T. Verts

Truth Table for AND (three inputs)

A	B	C	AND
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

©2014 Dr. William T. Verts

What About...

- If we can describe the behavior of AND...
- ...can we also describe OR?
- Yes, but there's a catch:
- The OR we use in English is not the same as the OR we use in computer logic!

©2014 Dr. William T. Verts

The OR in English

- "I am going to the store OR going to the beach."
- If I don't do either, I've lied,
- if I do one or the other, I've told the truth,
- but *if I do both I've lied!*
- In English the inference is that if I say I'll do one thing or the other, I won't do both!
- This is called an **Exclusive OR** (aka **XOR**).

©2014 Dr. William T. Verts


The OR we use in Logic

- If one input or the other is true, the output is true,
- If both inputs are true, the output is still true,
- This is called an **Inclusive OR**.

©2014 Dr. William T. Verts

When does Water flow?


- When either or both valves are open

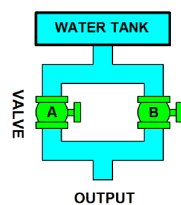

©2014 Dr. William T. Verts

When does the light come on?

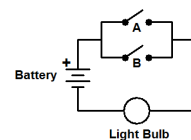- When either or both switches are closed



©2014 Dr. William T. Verts

Truth Table(s) for OR

A	B	XOR	A	B	OR
0	0	0	0	0	0
0	1	1	0	1	1
1	0	1	1	0	1
1	1	0	1	1	1

©2014 Dr. William T. Verts

General Rules for AND and OR

- AND: The output is 1 if all inputs are 1, the output is 0 if any input is 0.
- OR: The output is 1 if any input is 1, the output is 0 if all inputs are 0.
- XOR: The output is 1 if the inputs differ, the output is 0 if the inputs are the same.

©2014 Dr. William T. Verts

NOT

- "I am NOT going to the store."

A	NOT
0	1
1	0


©2014 Dr. William T. Verts

Gates

- A Gate is:
 - A **mathematical abstraction** for...
 - ...a **physical device** that...
 - ...implements the function of a **Truth Table**.


©2014 Dr. William T. Verts

AND, OR, and XOR gates

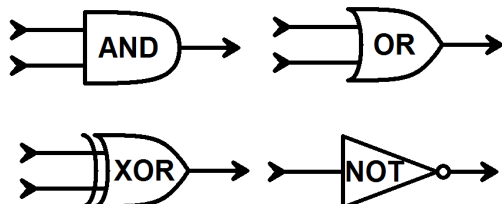


©2014 Dr. William T. Verts

NOT-OR = NOR

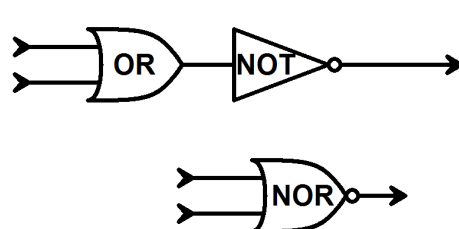


©2014 Dr. William T. Verts

NOT-AND = NAND

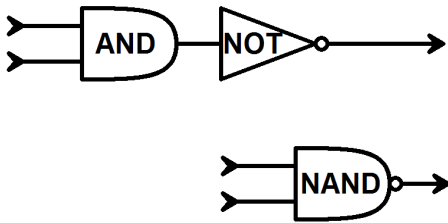


©2014 Dr. William T. Verts

What Does it Do?

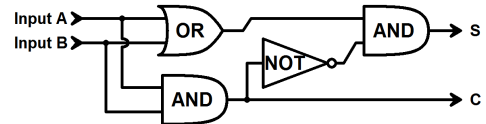


©2014 Dr. William T. Verts

Inputs 0,0

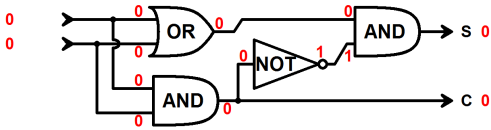


©2014 Dr. William T. Verts

Inputs 1,0

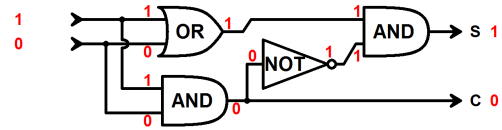


©2014 Dr. William T. Verts

Inputs 0,1

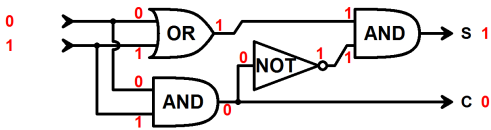

©2014 Dr. William T. Verts

Inputs 1,1

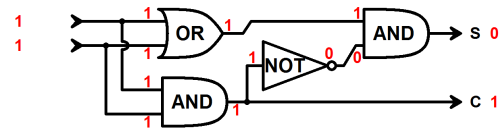

©2014 Dr. William T. Verts

What is its Function?

A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

©2014 Dr. William T. Verts

A Binary Adder!

A	B	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

©2014 Dr. William T. Verts